

436/Phs.(O)

UG/3rd Sem/PHY-H-CC-T-07/23

U.G. 3rd Semester Examination - 2023

PHYSICS

[HONOURS]

Course Code : PHY-H-CC-T-07

(Digital Systems and Applications)

[Old Syllabus]

Full Marks : 40

Time : 2½ Hours

The figures in the right-hand margin indicate marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP-A

1. Answer any **five** questions: $2 \times 5 = 10$

- a) Why binary number system is used in digital computation?
- b) Distinguish between sequential and combinational logic systems.
- c) Construct a single bit comparator using basic logic gates.
- d) Explain the given instruction for 8085 μP "STA E029H".

[Turn over]

- e) What do you mean by BCD? Explain with an example.
- f) Design an Ex-OR gate using NAND gates only.
- g) Prove the Boolean identity $AB + \bar{A}B + A\bar{B} = \bar{A} + B$.
- h) Which features of electrical signals can be measured by a CRO?

GROUP-B

2. Answer any two questions: 5×2=10

a) i) Convert the Boolean expression $Y = A.B.\bar{C} + A.\bar{B}C + \bar{A}BC$ into sum of products (SOP) form.

ii) Using a Karnaugh map, simplify the above Boolean expression for Y. Implement the simplified expression for Y using basic logic gates. 2+(2+1)

b) i) Distinguish between a flip-flop and a latch.

ii) Draw the circuit diagram of a 4-bit parallel-in serial-out shift register and explain its operation. 1+4

c) i) What do you mean by 8-bit microprocessor?

ii) Explain the functions of accumulator, stack-pointer, program counter and interrupt of 8085 microprocessor. 1+4

d) i) Describe the main features that differentiate synchronous from asynchronous sequential logic system.

ii) Explain the operation of decade counter and sketch its timing diagram. 1+(3+1)

GROUP-C

3. Answer any two questions: 10×2=20

a) i) Distinguish between RAM and ROM. What is memory mapping in computer architecture?

ii) Sketch the circuit realization of a clocked SR flip-flop with NAND gates. Explain its operation with truth table.

iii) How a JK flip-flop is converted into D-type and T-type flip-flop? (2+2)+(2+2)+2

b) i) Define deflection sensitivity of a CRO. Derive an expression for the same.

ii) Write down the truth table of a full adder. How will you arrange two half adders to construct a full adder? Explain. (1+4)+(2+3)

c) i) What is multiplexer? Construct a 4:1 multiplexer with basic logic gates and explain its operation. How many selection inputs are required for 32:1 multiplexer?

ii) Consider, there are three doors in a room. You want to set an electrical alarm that will buzz if anyone opens more than one door simultaneously. Construct a truth table and a Boolean expression for that logic. Implement that in a logic circuit.

(1+3+1)+(1+1+3)

d) i) What is assembly language for a microprocessor? Draw the timing diagram for the instruction MOV A,B in 8085 μP .

ii) Simplify the Boolean expression $\overline{\overline{A+B} + \overline{\overline{A+B}}}$. What is inequality detector in digital electronics? Explain its operation with logic circuit.

(2+3)+(2+1+2)